

# Complex Digital Design

## Final Lab Report

Junhan Bao, Wentai Ye

March 10, 2024

# 1 Summary

In the final project, we designed a 128-bit adder with a 3-layer structure, and it takes 5 clock cycles to complete a 512-bit addition. Besides, we designed a 512-bit subtractor, a 512-bit comparator and a function selector. The function selector can select the operation of addition, subtraction or comparison.

## 2 Technical Description

### 2.1 Function Selector

Based on the `uart_top` in Lab2, we added a function selection module because we can now operate subtraction and comparison besides addition. The final state machine diagram of `uart_top` is as figure[1]. The final state machine diagram of the 512-bit calculator in the above diagram is as figure[2].

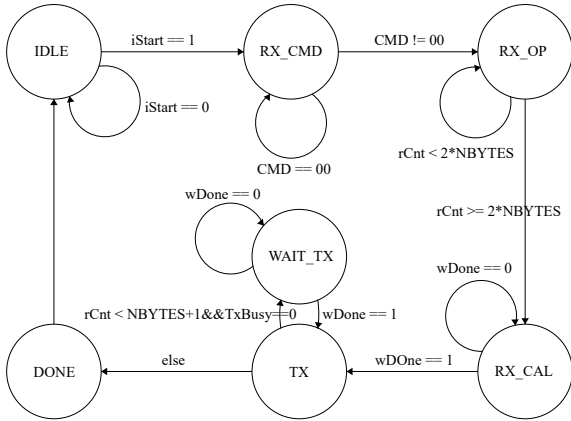


Figure 1: The state machine diagram of `uart_top`

It first compares the two input operands ( $iA$  and  $iB$ ); if  $iA$  is equal to  $iB$ , we can derive the sum or difference of the two operands, which is zero without any calculation. If  $iA$  is larger than  $iB$ , we can derive the sum or difference of the two operands by adding  $iA$  and the complement of  $iB$ .

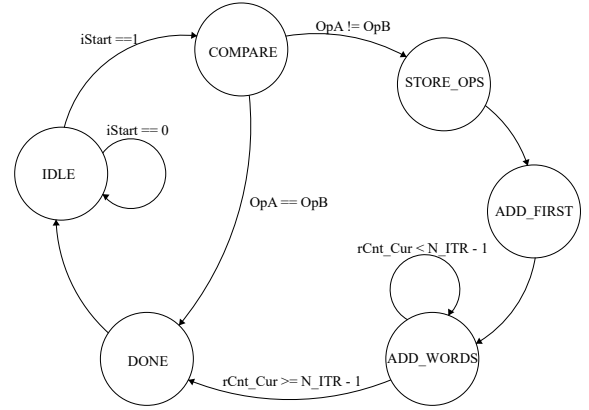


Figure 2: The state machine diagram of 512-bit calculator

### 2.2 Adder

#### 2.2.1 3-layer adder structure

We designed a 128-bit adder, where the bottom-level module is an 8-bit carry-lookahead adder. First, it is expanded to 32 bits through four layers of carry-select adders and then expanded to 128 bits through four more layers of carry-select adders.

The structure of the top layer is shown in figure[3]. The structure of the medium layer is shown in figure[4]. The structure of the bottom layer (Improved 8-bit carry-lookahead adder) is shown in figure[5].

 


Figure 3: The top layer structure of carry-select adder

If speed is the primary concern, a different design may be more appropriate. If the area is the primary concern, a smaller adder with fewer layers may be better. However, the design we have chosen is a good compromise between speed and area.

 


Figure 4: The medium layer structure of carry-select adder

 


Figure 5: The bottom layer structure of 8-bit carry-look-ahead adder

## 2.3 Subtractor

The 512-bit subtractor takes two 512-bit inputs,  $iA$  and  $iB$ , and produces a 512-bit output by first calculating the complement of the smaller operand, denoted as  $iA$ . The result is obtained by adding the complement of  $iA$  and the other operand  $iB$  using the adder that has been designed.

## 2.4 Comparator

The 512-bit comparator takes in two 512-bit inputs,  $iA$  and  $iB$ , and outputs a 3-bit result,  $oRes$ .

The comparator first computes the bitwise XOR (diff) of the two inputs. It then generates two sets of flags (L1 and L2) by checking if any of the 8-bit chunks in the diff are non-zero.

Next, the comparator selects the largest non-zero flag and corresponding 8-bit chunk in the L2 buffer and saves it in L1buff. The corresponding 64-bit chunk in input  $iA$  is also saved in Abuff.

The comparator then selects the largest non-zero flag and corresponding 8-bit chunk in the

L1buff and saves it in Asub. The comparator then processes the bits in Asub and L1buff to generate smaller 4-bit and 2-bit flags, and corresponding chunks ( $A4$ ,  $L4$ ,  $A2$ ,  $L2$ ) until only 1-bit flags ( $A1$ ,  $L1$ ) remain.

Finally, the comparator checks the value of L2 to determine the result. If all flags are zero,  $oRes$  is set to  $3'b010$ , indicating that the two inputs are equal. If the largest flag in  $iA$  is zero,  $oRes$  is set to  $3'b100$ , indicating that  $iA$  is larger than  $iB$ . Otherwise,  $oRes$  is set to  $3'b100$ , indicating that  $iA$  has a smaller value than  $iB$ .

# 3 Performance Evaluation

## 3.1 Timing

As shown in the figure[6] of the timing report below, the worst negative slack(WNS) of setup time(WHS) is 0.940 ns, and the worst hold slack is 0.115 ns. The worst delay is 6.840 ns, shown in figure[7].

Setup		Hold		Pulse Width	
Worst Negative Slack (WNS)	0.940 ns	Worst Hold Slack (WHS)	0.115 ns	Worst Pulse Width Slack (WPWS)	3.500 ns
Total Negative Slack (TNS)	0.000 ns	Total Hold Slack (THS)	0.000 ns	Total Pulse Width Negative Slack (TPWS)	0.000 ns
Number of Failing Endpoints:	0	Number of Failing Endpoints:	0	Number of Failing Endpoints:	0
Total Number of Endpoints:	9303	Total Number of Endpoints:	9303	Total Number of Endpoints:	4250

All user specified timing constraints are met.

Figure 6: TimingClosure of the Adder

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay
Path 1	1.024	8	9	33	design_1_iu_q_reg[65]C	design_1_iu_q_out_reg[D	6.840	1.641	5.199
Path 2	1.024	8	9	33	design_1_iu_q_reg[65]C	design_1_iu_q_reg[480]D	6.840	1.641	5.199
Path 3	1.024	8	9	33	design_1_iu_q_reg[65]C	design_1_iu_q_reg[481]D	6.840	1.641	5.199

Figure 7: The worst delay is 6.840 ns

However, in our design, since a 512-bit comparator is also implemented and integrated with a 512-bit calculator, the 128-bit adder is not the slowest combinational circuit but the comparator. The adder's WNS is around 1.0 ns when the comparator is disabled.

It takes 5 clock cycles in total to realize a 512-bit adder and subtractor. One of 5 cycles is used for the comparator, and the rest of the 4 cycles is used for 129-bit add, as figure[8] and

 


Figure 8: The simulation result of calculator adding function

 


Figure 9: The simulation result of calculator subtraction function

figure[9] show. Another, if the command is "C", which means only to compare 2 inputs, it only takes one clock cycle instead, as shown in figure[10].

 


Figure 10: The simulation result of calculator comparing function

### 3.2 Utilization and Power

The 128-bit calculator used 2938 LUTs and 2598 FF in total, as shown in the following figure[11] of the utilization report. The 512-

Name	Slice LUTs (53200)	Slice Registers (106400)	F7 Muxes (26600)	Bonded IOB (125)	BUFCTRL (32)
Top	3061	5300	8	4	2
Debounce (Debounce_Switch)	8	19	0	0	0
uart_top	3053	5281	8	0	0
Calculator_512bit_INST (Calc...	2938	2598	8	0	0
UART_RX_INST (uart_rx)	30	36	0	0	0
UART_TX_INST (uart_tx)	46	27	0	0	0

Figure 11: The utilization of 512-bit calculator

bit comparator has used 524 LUTs, as shown in figure[12]. As for the power consumption, its total on-chip power is 0.135W at a medium confidence level, as shown in figure[13].

Name	Slice LUTs (53200)	Bonded IOB (125)
comparator_512bit	534	1027

Figure 12: The utilization of 512-bit comparator

 


Figure 13: The power report of this design

## 4 Comparison

Ripple carry adder with ADDER\_WIDTH = 16 takes 16 clock cycles in total as shown below. Though it consumes fewer hardware resources, it achieves fewer functions and worse performs.

The WNS is 2.559 ns for ripple adder, as shown below, which is quite a lot, which means it is still possible to make it calculator more bits every clock cycle, for example, 24 bits.

As shown in figure[16], the Ripple adder costs 1336 LUTs, as shown below. It is pretty much less than a 128-bit adder.

 


Figure 14: The simulation result of the 16-bit RippleAdder

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 2.559 ns	Worst Hold Slack (WHS): 0.132 ns	Worst Pulse Width Slack (WPWS): 3.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 6855	Total Number of Endpoints: 6855	Total Number of Endpoints: 4230

Figure 15: The timing closure of the 16-bit RippleAdder

Work	LUTs	WNS(ns)	Power	Required Clock Cycle
This Design	2938	0.940 ns	0.135W	5
16bit-Ripple Adder	1336	2.559 ns	0.145 W	16

Table 1: Comparasion between this design and 16-bit ripple adder

Name	^1	Slice LUTs (53200)	Slice Registers (106400)	Bonded IOB (125)	BUFGCTRL (32)
uart_top_2		1411	4229	4	1
mp_adder_INST (mp_adder)		1336	1574	0	0
UART_RX_INST (uart_rx)		26	36	0	0
UART_TX_INST (uart_tx)		42	27	0	0

Figure 16: The area cost of the 16-bit ripple adder

Compared to the ripple carrier adder, the adder we designed is much faster but larger with more functions. The reason is that the ripple carrier adder is a serial adder, but the adder we designed to put as much logic into parallel operation as possible. The ripple carrier adder needs to wait for the carry signal to be calculated before it can calculate the next bit. In contrast, this design can calculate multiple bits simultaneously, making it much faster. In addition, since more parallel modules are needed, this design costs more hardware resources.

As for the design of the carry-select adder, we found that it could perform best when 4 sub-adder blocks are implemented. If the number of sub-adder blocks goes up, it is better to use a varied-sized carry-select adder.

As for the design of the carry-lookahead adder, the more carries that are calculated beforehand, the more benefits we can gain on calculation speed. We also found that using a multi-input adder calculates faster than the combination of the 2-input adder.

As for an 8-bit carry-lookahead adder, the calculation of carry-out requires the largest amount of computation, performing an AND operation on 9 inputs and then performing an OR on 8 inputs. To reduce the delay caused by data passing through gates, we used multi-

input AND gates and multi-input OR gates to perform this operation.

Experimental results have shown that different implementation methods can result in variations in the logic gate generation and impact timing.

For example, when we need a 3-input AND operation, if we write "iA & iB & iC", two AND gates will be instantiated, resulting in a time delay caused by two AND gates. However, if we write "&iA, iB, iC", one 3-input AND gate will be instantiated, resulting in a time delay caused by only one 3-input AND gate. This causes its calculation speed to be much faster than that of two 2-input AND gates. Therefore, we used this characteristic when designing the carry-lookahead logic circuit to lower the calculation time significantly.

However, the situation does not get better as the input number increases. When it comes to 32 inputs, the speed of calculation gets slower, according to our experiments. Plus, since the 32-input carry-lookahead logic circuit is too long to write and difficult to debug, we did not try the carry-lookahead 32-bit adder.